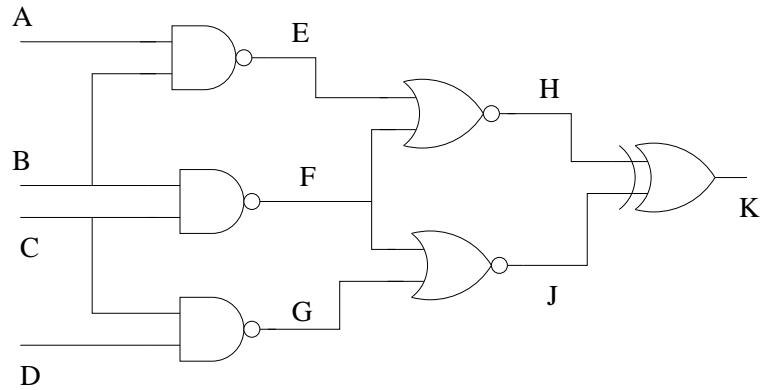


# EE709 Assignment


Madhav P. Desai

March 31, 2023

1. Consider the following logic network:



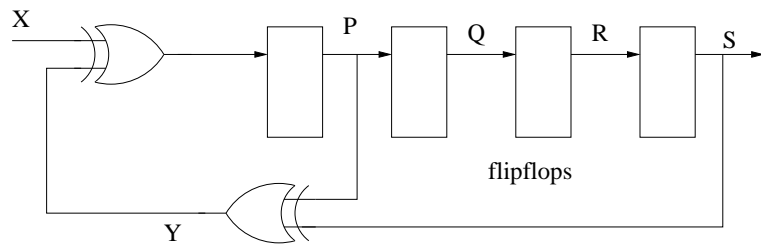- (a) Calculate a product of sums formula (CNF) which describes this network.
- (b) Using the minisat solver, find an input assignment such that the output  $K$  is 0.
- (c) Using the minisat solver, find an input assignment such that the output  $K$  is 1.
2. Consider the sequential machine shown below:



- (a) Suppose the machine starts in the state  $P = Q = R = S = 1$ . Using minisat, find a sequence of input values at  $X$  which will take the machine to the state  $P = Q = R = S = 0$ .